

Design and Implementation of VLSI Systems

Lecture04

MOSFET

MOS transistor theory


- Schedule for 4 lectures
 - Ideal (Shockley) Model
 - Non-ideal model
 - Inverter DC characteristics
 - SPICE

gate-oxide-body sandwich = capacitor



Operating modes

- Accumulation
- Depletion
- Inversion

 - The charge accumulated is proportional to the excess gate-channel voltage ($V_{gc} - V_t$)



Gate capacitance as a function of V_{GS}

  

The MOS transistor has three regions of operation

- Cut off

$$V_{gs} < V_t$$

- Linear (resistor):


$$V_{gs} > V_t \text{ \& } V_{ds} < V_{SAT} = V_{gs} - V_t$$

Current prop to V_{ds}

- Saturation:

$$V_{gs} > V_t \text{ and } V_{ds} \geq V_{SAT} = V_{gs} - V_t$$


Current is independent of V_{ds}

 


NMOS transistor, 0.25 μ m, $L_d = 10\mu$ m, $W/L = 1.5$, $V_{DD} = 2.5$ V, $V_T = 0.4$ V

How to calculate the current value?

 - MOS structure looks like parallel plate capacitor while operating in inversion
 - Gate – oxide – channel
- $Q_{\text{channel}} = CV$
- $C = \epsilon_{\text{ox}} WL / t_{\text{ox}} = C_{\text{ox}} WL$ (where $C_{\text{ox}} = \epsilon_{\text{ox}} / t_{\text{ox}}$)
- $V = V_{\text{gc}} - V_{\text{t}} = (V_{\text{gs}} - V_{\text{ds}}/2) - V_{\text{t}}$



continuous
conductive
channel

 

Carrier velocity is a factor in determining the current

- Charge is carried by electrons
- Carrier velocity v proportional to lateral E-field between source and drain
- $v = \mu E$ μ called mobility
- $E = V_{ds}/L$
- Time for carrier to cross channel:
 $t = L / v$

$$I=Q/t$$

- Now we know
 - How much charge Q_{channel} is in the channel
 - How much time t each carrier takes to cross

$$I_{ds} = \frac{Q_{\text{channel}}}{t}$$

$$= \mu C_{\text{ox}} \frac{W}{L} \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$= \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

In linear mode ($V_{gs} > V_t$ & $V_{ds} < V_{gs} - V_t$)

$$I_{ds} = \frac{Q_{\text{channel}}}{t}$$

$$= \mu C_{\text{ox}} \frac{W}{L} \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$= \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

Can be ignored for small V_{ds}


$$I_{ds} = \beta \left((V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right)$$

$$I_{ds} = \beta (V_{gs} - V_t) V_{ds}$$

➤ For a given V_{gs} , I_{ds} is proportional (linear) to V_{ds}

In saturation mode ($V_{gs} > V_t$ and $V_{ds} \geq V_{gs} - V_t$)
 
$$\begin{aligned} I_{ds} &= \frac{Q_{\text{channel}}}{t} \\ &= \mu C_{\text{ox}} \frac{W}{L} \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} \\ &= \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} \\ I_{ds} &= \beta \left(V_{gs} - V_t - \frac{V_{dsat}}{2} \right) V_{dsat} \\ &= \frac{\beta}{2} (V_{gs} - V_t)^2 \end{aligned}$$



➤ Now drain voltage no longer increases current

Operation modes summary

 


FIG 2.7 I-V characteristics of ideal nMOS transistor

 


FIG 2.8 I-V characteristics of ideal pMOS transistor

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

CURRENT-VOLTAGE RELATIONS

$$\beta = \mu C_{\text{ox}} \frac{W}{L}$$

β : transconductance parameter of transistor

W/L : width-to-length ratio

- As W increases, more carriers available to conduct current.
- As L increases, V_{ds} diminishes in effect (more voltage drop) \rightarrow takes longer to push carriers across the transistor \rightarrow reducing current flow.

Transistor capacitance

 


FIG 2.10 Overlap capacitance


 
 


FIG 2.14 Capacitances of an MOS transistor


- Gate capacitance: to body + to drain + to source
- Diffusion capacitance: source-body and drain-body capacitances

Gate capacitance as a function of V_{GS}

 


Source/Drain diffusion capacitance

 - C_{sb} , C_{db}
- Undesirable, called *parasitic* capacitance
- Capacitance depends on area and perimeter
 - Use small diffusion nodes
 - Comparable to C_g
 - Varies with process



$$\begin{aligned} C_{diff} &= C_{bottom} + C_{sw} = C_j \times AREA + C_{jsw} \times PERIMETER \\ &= C_j L_S W + C_{jsw} (2L_S + W) \end{aligned}$$

SUMMARY OF SHOCKLEY MODEL

 

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

 


FIG 2.7 I-V characteristics of ideal nMOS transistor

for nMOS

$$\beta = \beta_n = \mu_n \frac{\epsilon_{ox} W}{t_{ox} L}$$

$$V_t = V_{tn}$$

for pMOS



$$\beta = \beta_p = \mu_p \frac{\epsilon_{ox} W}{t_{ox} L}$$

$$V_t = V_{tp}$$



$$\mu_p < \mu_n (\mu_n \approx 2 \times \mu_p)$$

Covered ideal (long channel) operation (Shockley model) of transistor

IDEAL VS. NON-IDEAL

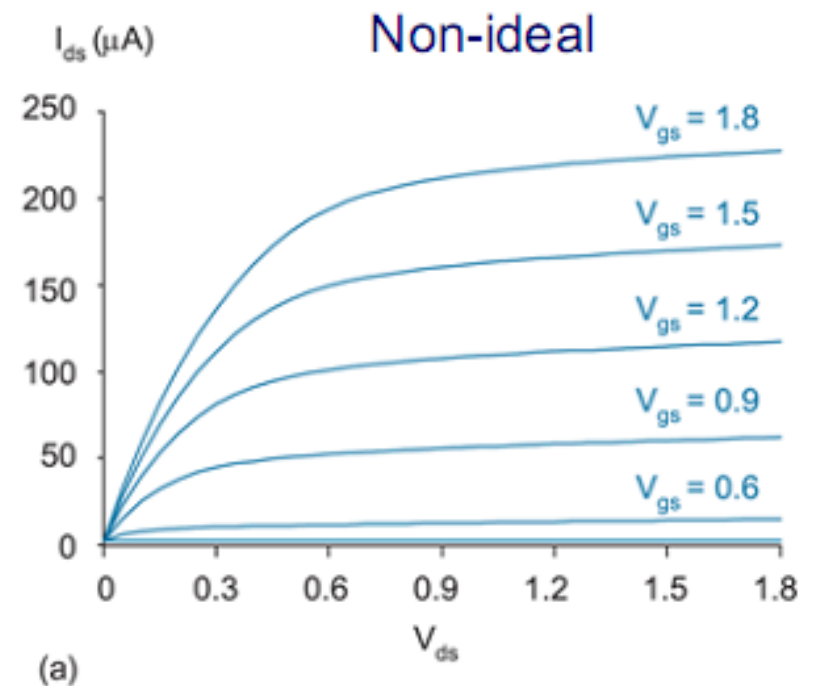 

  - Saturation current does not increase quadratically with V_{gs}
- Saturation current lightly increases with increase in V_{ds}



- There is leakage current when the transistor is in cut off
- I_{ds} depends on the temperature

VELOCITY SATURATION

At high electric field, drift velocity rolls off due to carrier scattering


$$\begin{aligned}v &= \mu_n E \text{ for } E \leq E_c \\ &= v_{sat} = \mu_n E_c \text{ for } E \geq E_c\end{aligned}$$

$$\begin{aligned}I_{ds} &= \mu C_{ox} \frac{W}{L} \frac{V_{gs} - V_t}{2} V_{ds} \\ I_{ds} &= C_{ox} W \frac{V_{gs} - V_t}{2} v_{SAT}\end{aligned}$$

Empirically:

$$I_{ds} \propto (V_{gs} - V_t)^\alpha$$

where α is close to 1

 

ALPHA MODEL

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ I_{dsat} \frac{V_{ds}}{V_{dsat}} & V_{ds} < V_{dsat} & \text{linear} \\ I_{dsat} & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

$$I_{dsat} = P_c \frac{\beta}{2} (V_{gs} - V_t)^\alpha$$

$$V_{dsat} = P_v (V_{gs} - V_t)^{\alpha/2}$$

 


FIG 2.17 I-V characteristics for nMOS transistor with velocity saturation

P_c , P_v and α are found by fitting the model to the empirical modeling results

CHANNEL LENGTH MODULATION

- The reverse-bias p-n junction between drain and body forms a depletion region with a width L_d that increases with V_{db}

$$L = L - L_d$$

- Increasing V_{ds}
 - increases depletion width
 - decreases effective channel length
 - increases current

$$I_{ds} = \beta \frac{(V_{gs} - V_t)^2}{2} (1 + \lambda V_{ds})$$

Channel length modulation factor (empirical factor)


 
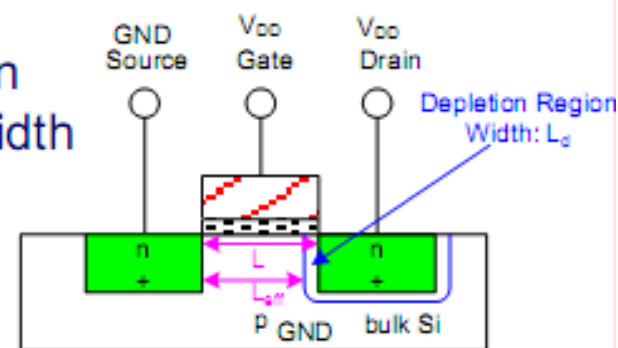


FIG 2.18 I-V characteristics of nMOS transistor with channel length modulation

LEAKAGE CURRENT: SUBTHRESHOLD

 

Junction leakage

□ Subthreshold leakage is the biggest source in modern transistors

$$I_{ds} = I_{ds0} e^{\frac{V_{gs} - V_t}{nV_T}} \left(1 - e^{\frac{-V_{ds}}{V_T}} \right)$$

$$I_{ds0} = \beta v_T^2 e^{1.8} \quad n = 1.4-15$$

Boltzmann distribution

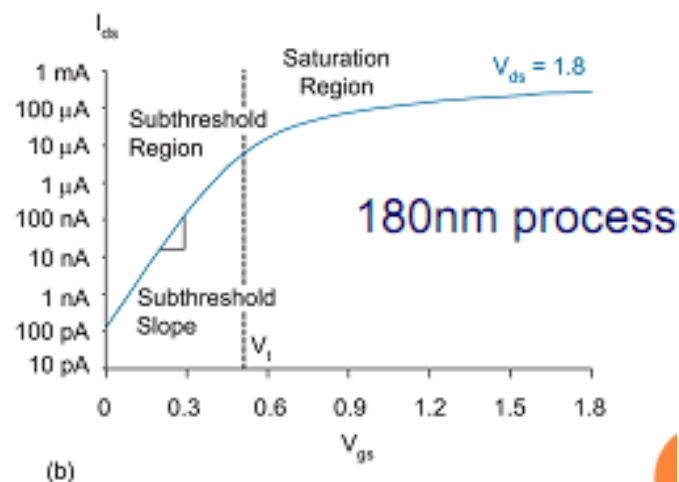
 



FIG 2.15 Simulated I-V characteristics

LEAKAGE CURRENT: JUNCTION LEAKAGE AND TUNNELING

Junction leakage: reverse-biased p-n junctions have some leakage.


I_s depends on doping levels and area and perimeter of diffusion regions
 
$$I_D = I_s \left(e^{\frac{V_D}{V_T}} - 1 \right)$$



Tunneling leakage:

 - Carriers may tunnel through very thin gate oxides
 - Negligible for older processes
- (and future processes with high-k dielectrics!)



IMPACT OF TEMPERATURE

 


FIG 2.21 I-V characteristics of nMOS transistor in saturation at various temperatures

 


FIG 2.22 I_{dsat} vs. temperature

- Carrier mobility decreases with $T^o \uparrow$
 - Threshold voltage decreases nearly linearly with $T^o \uparrow$
 - Junction leakage increases with $T^o \uparrow$
 - ON current decreases and OFF current increases with $T^o \uparrow$
- Circuit performance is generally worst at high $T^o \uparrow$
- *negative temperature coefficient*

IMPACT OF TEMPERATURE (CONT.)

Circuit performance can be improved by cooling

- Subthreshold leakage decreases with $T^{\circ}\downarrow$
- Velocity saturation increases with $T^{\circ}\downarrow \rightarrow$ more current
- Mobility increases with $T^{\circ}\downarrow \rightarrow$ save power
- Depletion regions become wider with $T^{\circ}\downarrow \rightarrow$ less junction capacitance

BODY EFFECT

- V_t is sensitive to V_{sb} -> *body effect*

$$V_t = V_{t0} + \gamma \left(\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s} \right)$$


$$\phi_s = 2v_T \ln \frac{N_A}{n_i}$$

$$\gamma = \frac{t_{ox}}{\epsilon_{ox}} \sqrt{2q\epsilon_{si}N_A} = \frac{\sqrt{2q\epsilon_{si}N_A}}{C_{ox}}$$


- What is the impact on V_t if we increase/decrease the body bias?

PROCESS VARIATIONS

 Both MOSFETs have 30nm channel with 130 dopant atoms in the channel depletion region



threshold voltage 0.97V

 

threshold voltage 0.57V

Process variations impact gate length, threshold voltage, and oxide thickness

SUMMARY OF TRANSISTOR OPERATION

 


FIG 2.7 I-V characteristics of ideal nMOS transistor

 



FIG 2.8 I-V characteristics of ideal pMOS transistor

DC RESPONSE

○ DC Response: V_{out} vs. V_{in} for a gate

○ Ex: Inverter

- When $V_{in} = 0 \rightarrow V_{out} = V_{DD}$
- When $V_{in} = V_{DD} \rightarrow V_{out} = 0$
- In between, V_{out} depends on transistor size and current
- By KCL, must settle such that $I_{dsn} = |I_{dsp}|$
- We could solve equations
- But graphical solution gives more insight

 


TRANSISTOR OPERATION

- Current depends on region of transistor behavior
- For what V_{in} and V_{out} are nMOS and pMOS in
 - Cutoff?
 - Linear?
 - Saturation?

NMOS OPERATION

Cutoff	Linear	Saturated
$V_{gsn} < V_{thn}$	$V_{gsn} > V_{thn}$ $V_{dsn} < V_{gsn} - V_{thn}$	$V_{gsn} > V_{thn}$ $V_{dsn} > V_{gsn} - V_{thn}$

 


PMOS OPERATION

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$


$$V_{tp} < 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

 


I-V CHARACTERISTICS

- Make pMOS is wider than nMOS such that $\beta_n = \beta_p$

 


CURRENT VS. V_{OUT} , V_{IN}

 


LOAD LINE ANALYSIS

- For a given V_{in} :
 - Plot I_{dsn} , I_{dsp} vs. V_{out}
 - V_{out} must be where |currents| are equal in

 



LOAD LINE ANALYSIS

$$V_{in} = V_{DD}$$

 

DC TRANSFER CURVE

 
 
- Transcribe points onto V_{in} vs. V_{out} plot



OPERATING REGIONS


- Revisit transistor operating regions

Region	nMOS	pMOS
A		
B		
C		
D		
E		

  


BETA RATIO

 - If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- Called *skewed* gate
- Other gates: collapse into equivalent inverter




NOISE MARGINS

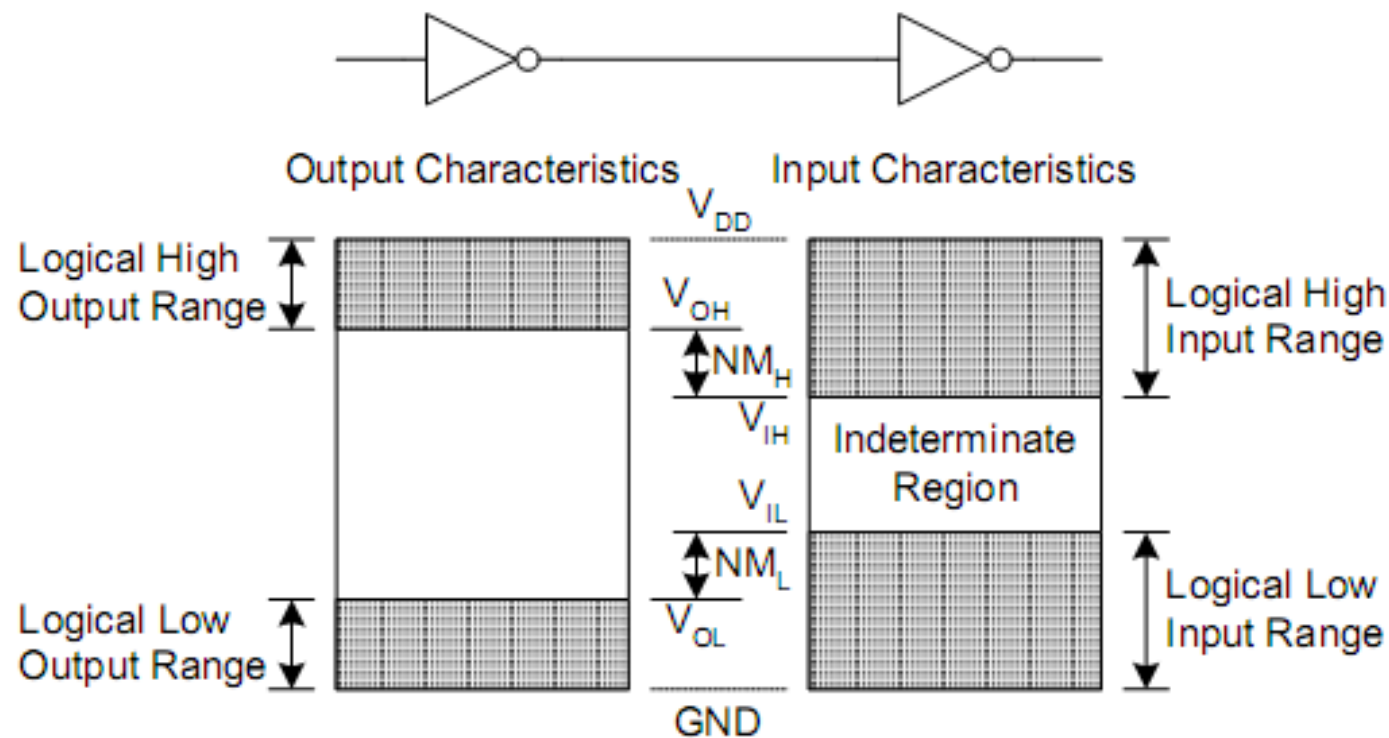- How much noise can a gate input see before it does not recognize the input?



LOGIC LEVELS

 - To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristic




TRANSIENT RESPONSE




- *DC analysis* tells us V_{out} if V_{in} is constant
- *Transient analysis* tells us $V_{\text{out}}(t)$ if $V_{\text{in}}(t)$ changes
 - Requires solving differential equations
- Input is usually considered to be a step or ramp
 - From 0 to V_{DD} or vice versa

PASS TRANSISTORS


- We have assumed source is grounded
- What if source > 0 ?
 - e.g. pass transistor passing V_{DD}
- $V_g = V_{DD}$
 - If $V_s > V_{DD} - V_t$, $V_{gs} < V_t$
 - Hence transistor would turn itself off
- nMOS pass transistors pull no higher than $V_{DD} - V_{tn}$
 - Called a degraded “1”
 - Approach degraded value slowly (low I_{ds})
- pMOS pass transistors pull no lower than V_{tp}
- Transmission gates are needed to pass both 0 and 1

 

PASS TRANSISTOR CKTS

   

PASS TRANSISTOR DC CHARACTERISTICS

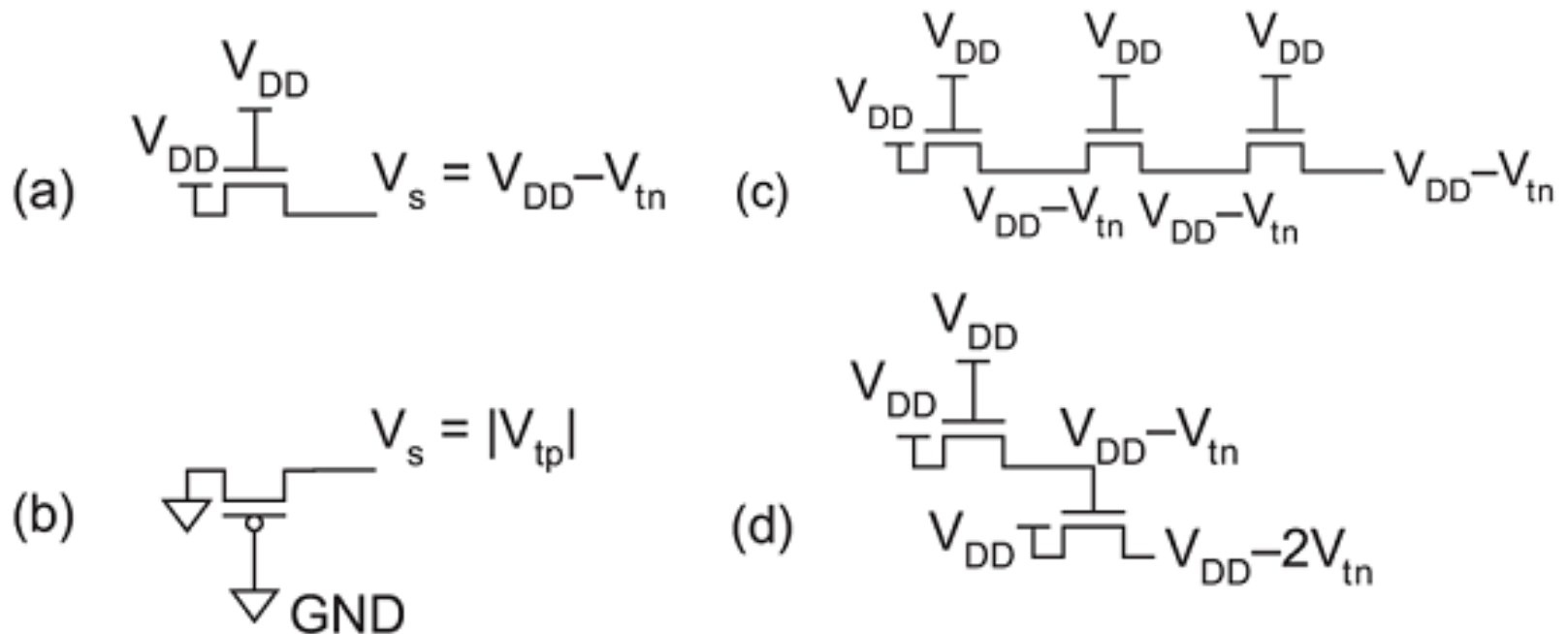

- As the source can rise to within a threshold voltage of the gate, the output of several transistors in series is no more degraded than that of a single transistor

Summary

- Covered ideal (long channel) operation (Shockley model) of transistor
- Short-channel transistors
- TA