 


Design and Implementation of VLSI Systems

Lecture02

CMOS logic

Impact of doping on silicon resistivity




silicon

 
4.995×10^{22} atoms in cm^3

Resistivity $3.2 \times 10^5 \Omega\text{cm}$


dope with
phosphorous
or arsenic \rightarrow
n-type



dope with
boron \rightarrow
p-type

 

 
1 atom in billion \Rightarrow
1 atom in million \Rightarrow
1 atom in thousand \Rightarrow



1 atom in billion \Rightarrow
1 atom in million \Rightarrow
1 atom in thousand \Rightarrow

\Rightarrow Electrons are more mobile/faster than holes


What happens if we sandwich p & n types?

 


Anode Cathode



FIG 1.7 p-n junction diode structure and symbol



 


One-dimensional representation

 

- In equilibrium, the drift and diffusion components of current are balanced; therefore the net current flowing across the junction is zero.

PN-junction regions of operation

   


In reverse bias, the width of the depletion region increases. The diode acts as voltage-controlled capacitor.

A forward bias decreases the potential drop across the junction. As a result, the magnitude of the electric field decreases and the width of the depletion region narrows.

nMOS and pMOS transistors



Each transistor consists of a stack of a conducting gate, an insulating layer of silicon dioxide and a semiconductor substrate (body or bulk)

nMOS transistor

 


$g = 0$

$g = 1$

  

pMOS transistor

 

$g = 0$




$g = 1$



Body is typically grounded

Body is typically at supply voltage

nMOS transistor

 


$g=0$: When the gate is at a low voltage ($V_{GS} < V_{TN}$):





- p-type body is at low voltage
- source and drain-junctions diodes are OFF
- transistor is OFF, no current flows

$g=1$: When the gate is at a high voltage ($V_{GS} \geq V_{TN}$):

 - negative charge attracted to body
- inverts a channel under gate to n-type
- transistor ON, current flows, transistor can be viewed as a resistor



nMOS pass '0' more strongly than '1'

    


Input $g = 1$ Output
 $0 \rightarrow$ strong 0

$g = 1$
 $1 \rightarrow$ degraded 1

- Why does '1' pass degraded?

$$V_s = V_{DD} - V_{tn}$$

pMOS transistor

 





$g=0$: When the gate is at a low voltage ($V_{GS} < V_{TP}$):

- positive charge attracted to body
- inverts a channel under gate to p-type
- transistor ON, current flows

$g=1$: When the gate is at a high voltage ($V_{GS} \geq V_{TP}$):

- negative charge attracted to body
- source and drain junctions are OFF
- transistor OFF, no current flows


pMOS pass '1' more strongly than '0'

    

Input $g = 0$ Output
 $0 \rightarrow \text{degraded } 0$

$g = 0$
 $1 \rightarrow \text{strong } 1$

- Why does '0' pass degraded?

 

An nMOS and pMOS make up an inverter


 



FIG 1.10 Inverter schematic (a) and symbol (b) $Y = \overline{A}$

pMOS + nMOS = CMOS


More CMOS gates

 

What is this gate function?

 

$$Y = \overline{A \bullet B}$$

 

What's wrong about this design?

3-input NANDs

 


FIG 1.12 3-input NAND gate schematic
 $Y = \overline{A \bullet B \bullet C}$

 


FIG 1.13 General logic gate using pull-up and pull-down networks

If: Pull up network = 1 \Rightarrow pull down network must = 0

If: Pull up network = 0 \Rightarrow pull down network must = 1

3-input NANDs

What are the advantages of CMOS circuit style?

Series-Parallel Combinations


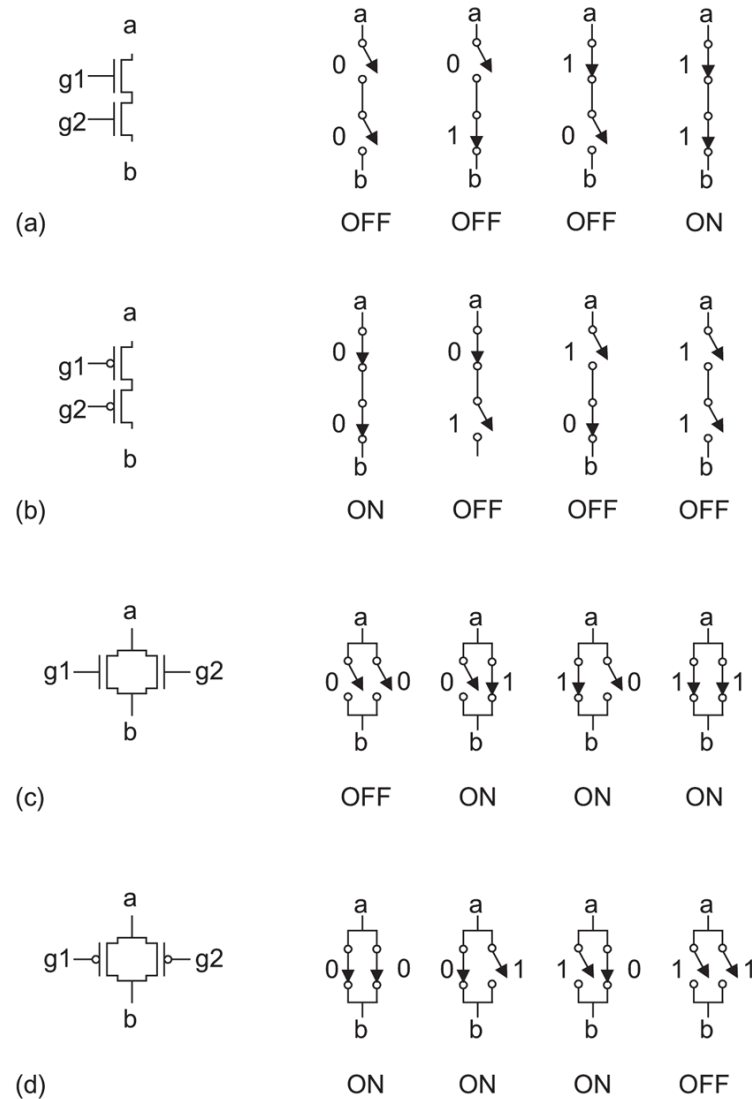
 


FIG 1.14 Connection and behavior of series and parallel transistors

 What are the transistor schematics of the NOR gate?



And-Or-Inverter (AOI) gate


 
 
 


FIG 1.17 CMOS compound gate for function $Y = \overline{(A \bullet B) + (C \bullet D)}$

 

CMOS gate design steps

Steps:

- Design pull down network
 - Use the inverse of the given function
 - NMOS circuit
- Design pull up network
 - Use the opposite network of the pull down network: parallel - serial; serial – parallel
 - PMOS circuit
- Combine 2 networks

Examples

Example 1.2

Sketch a static CMOS gate computing $Y = (A + B + C) \cdot D$

Transmission gate

 


FIG 1.24 Tristate buffer symbol

FIG 1.20 Transmission gate

Tri-state inverter



 


FIG 1.26 Tristate inverter

Multiplexer (MUX)

 

(a)

 

(b)

FIG 1.27 Transmission gate multiplexer

Latch design


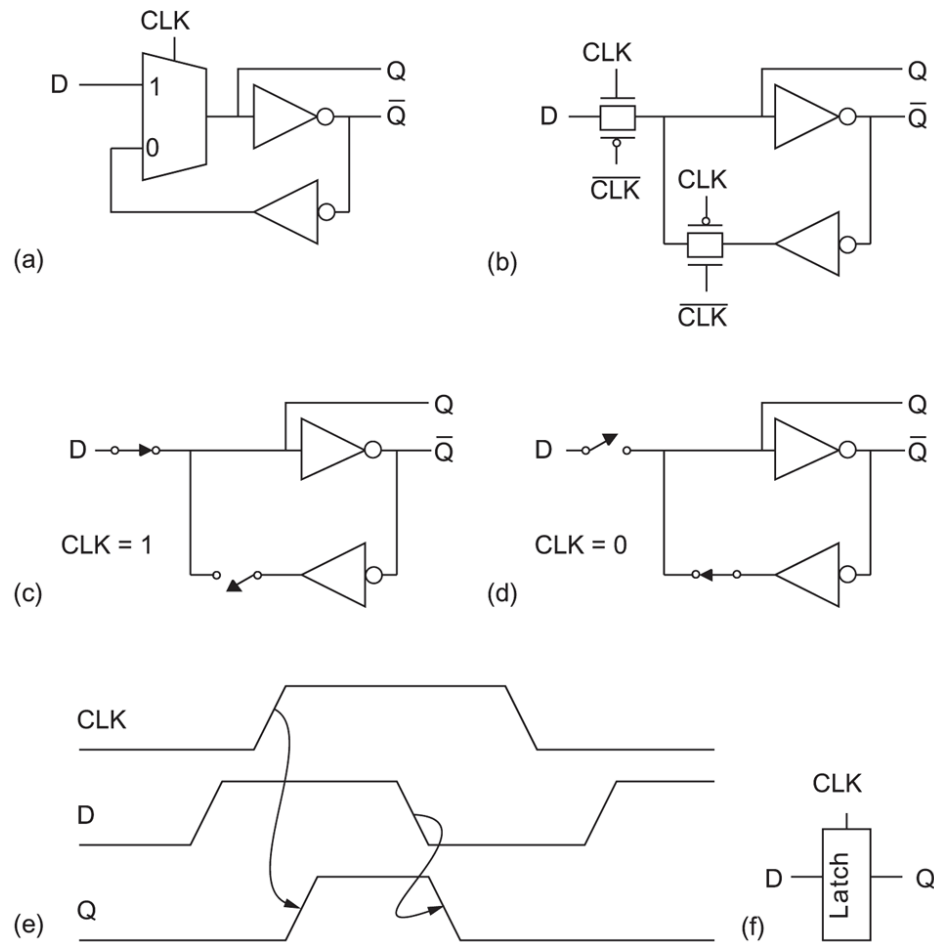
 
 
 
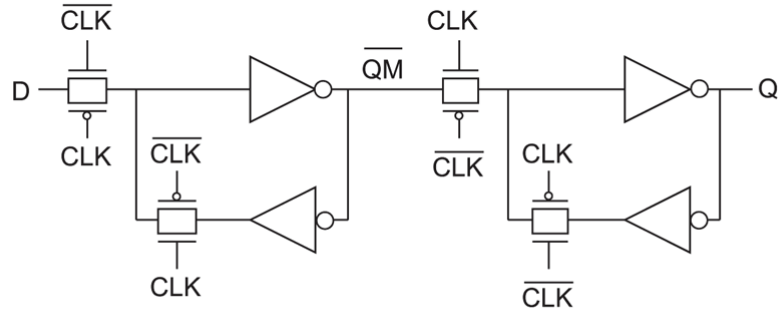
 


FIG 1.30 CMOS positive-level-sensitive D latch

Flip-flop (edge triggered) design

 

Summary

- Introduction to VLSI systems and the semiconductor industry
- Basic overview of pn junctions and MOS transistors
- Designing digital logic gates using transistors